

## **EXPERIMENT NUMBER-01(a)**

### **AIM:-**

Solution of First Order Differential Equations(L-R Circuit).

### **APPARATUS REQUIRED:-**

- Scilab

### **PROGRAMMING CODE:-**

```
clc;
clear;
disp("Prattayaya amrit")
disp("13601")
disp("B.Sc(Hons) Electronics")
disp("AIM :- Solution of First Order Differential Equation of LR
circuit ")
//taking input from the user
L = input("Enter the value of Inductor (in Henry) : ")
R = input("Enter the value of Resistor (in Ohm) : ")
V = input("Enter the value of Peak Value (in Volt) : ")
f = input("Enter the value of Frequency (in Hertz) : ")
//defining a function to solve ordinary differential equation
function idot=F(t, i, Vin, R, L)
    idot = (V*sin(2*pi*f*t) - i*R)/L
endfunction
i0 = 0;
t0 = 0;
t = 0 : 0.01/f : 10/f;
i = ode(i0, t0, t, F);
clf;
plot(t, i, "color", "black")
// to add legend, title and axis labels
xlabel("Time (in sec)")
ylabel("First Order Differential Equation")
title("AIM :- Solution of First Order Differential Equation")
legend("Inductor")
```

## OUTPUT:-

```
"Prattayaya amrit"  
"13601"  
"B.Sc(Hons) Electronics"  
"AIM :- Solution of First Order Differential Equation of LR circuit "  
Enter the value of Inductor (in Henry) : 12  
  
Enter the value of Resistor (in Ohm) : 23  
  
Enter the value of Peak Value (in Volt) : 15  
  
Enter the value of Frequency (in Hertz) : 100  
  
-->
```

